

Day 2: Nonlinear Effects.

Tube Screamer Clipping Circuit

New component Diode

New circuit analysis technique

Newton-Raphson Method.

JUCE, C++ implementations.

Linear vs. Nonlinear Effects.

Gain, DC

Distortion

EQ, Filter


Compression

Echo, Reverb

Start with digital then analog.

$$y = g * x + mu$$

Characteristic Curve

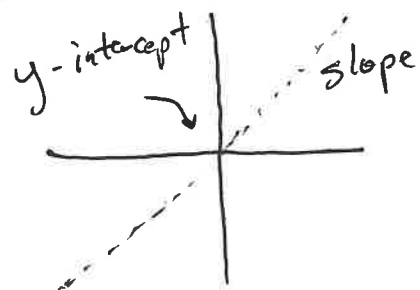

Linear operations result in straight line.

Nonlinear operations have a curve.

DC Sweep.

iZotope Trash 2

① ② Common types in audio

Full-wave rectification: $\text{abs}(\cdot)$

Half-wave rectification: diode

Hard-clipping, soft clipping



Cubic, arctan, tanh

Analog: diodes as a nonlinear component

Symbol



Basic idea current only flows in one direction.

With a resistor $V = IR$.






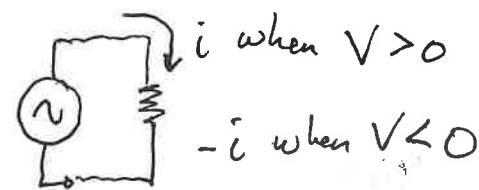
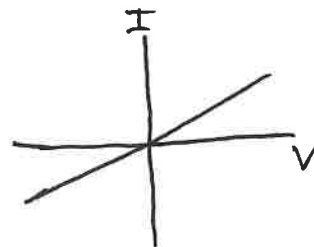


Diode is open circuit ($i=0$) when $V < 0$


Diode is short circuit when $V > 0$

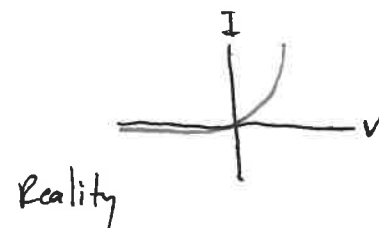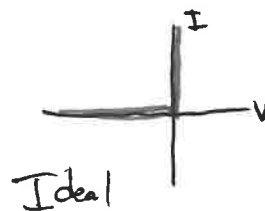

Ideal Diode Examples

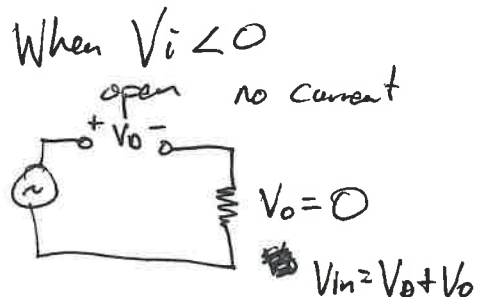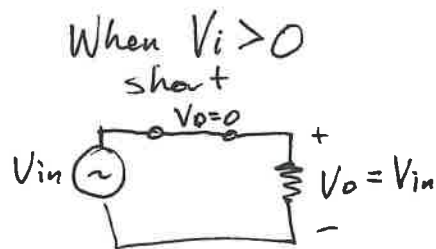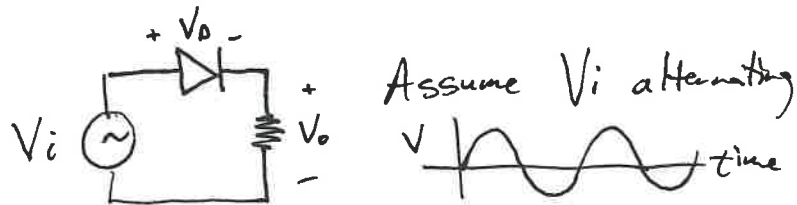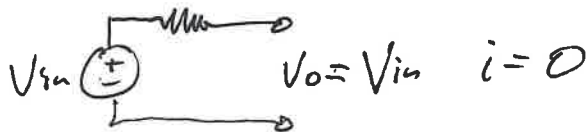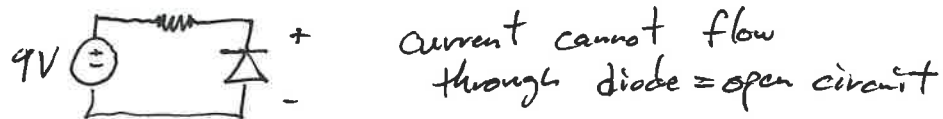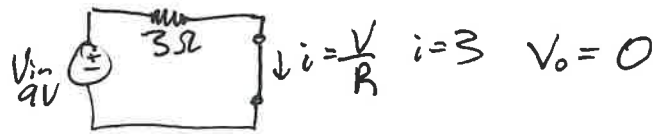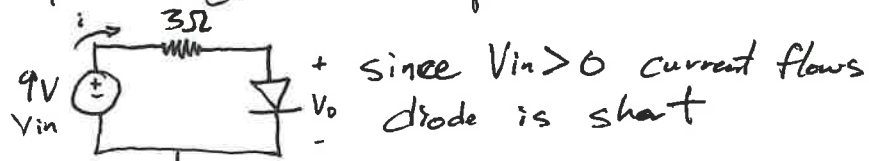


Half-wave Rectifier

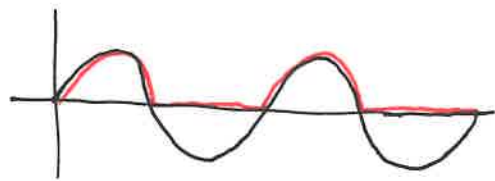

③ ④

More accurate model

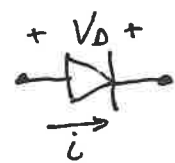

Shockley Diode Equation

↳ relationship between voltage & current

$$i = I_s \left(e^{\frac{V_o}{nV_T}} - 1 \right)$$

I_s - saturation current

V_T - thermal voltage

n - emission coefficient
"quality factor"

Note: different types of diodes can be modeled using different values.

Silicon vs. Germanium.




diodeEquation.m

⑦

Voltage where diode starts to conduct $V = 0.7$ silicon
 $V = 0.3$ germanium

Silicon	Germanium
$I_s = 10^{-12} - 10^{-15}$	10^{-6}
$n = 1$ ideal diode	$n = 1-2$ changes slope

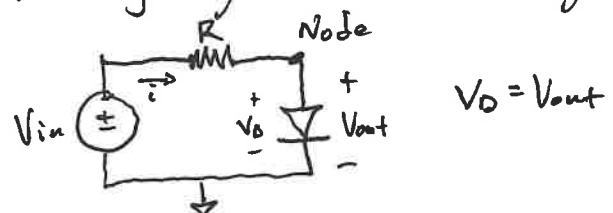Analyzing circuits using diode equation. ⑤



Currents into node = currents out

$$\frac{V_i - V_{out}}{R} = I_s \left(e^{\frac{V_{out}}{nV_T}} - 1 \right)$$

Assume V_i is known: input signal

Need to find V_{out} : output signal

Can we solve for V_{out} ?

$$\frac{V_i}{R} = I_s \left(e^{\frac{V_{out}}{nV_T}} - 1 \right) + \frac{V_{out}}{R}$$

We cannot factor out V_{out} . due to exponent

This is a special type of equation

called an "implicit equation"

Other type called "explicit equation"

↳ we could solve V_{out} as function of V_i .

Explicit equations can have "analytic" solution

Implicit equations ~~can~~ do not have analytic solution

instead we use "numerical solution"

↳ iterative process "guess and check"

⑥ Step back

Examples $y = mx + b$ $y = 5x + 2$

Explicit equation the thing we are trying to calculate "y" is isolated and there is only one of it.

More complicated. Solve for x

$$-1 = x^2 + 2x \text{ set equal to zero}$$

$$0 = x^2 + 2x + 1 \text{ can we factor?}$$

$$0 = (x+1)(x+1)$$

$$x = -1$$

Quadratic Equation $0 = ax^2 + bx + c$

$$x = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a} \quad \frac{-2 \pm \sqrt{2^2 - 4 \cdot 1 \cdot 1}}{2 \cdot 1} = \frac{-2 \pm \sqrt{0}}{2} = -1$$

Some equations cannot be broken down this way

$$0 = x^3 + 2x - 2 \text{ solve for "x"}$$

This is an implicit equation


No analytic solution

Use numerical, guess and check technique.


Matlab Plot $x = [-2 : .001 : 2]$

$\text{plot}(x, x.^3 + 2 \cdot x - 2);$

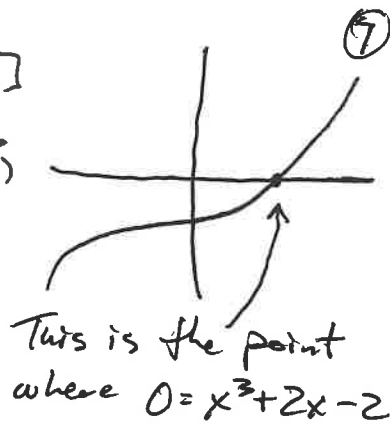In other words, this is the value of "x" that makes this equation true.




How do we find this? Gradual decent.

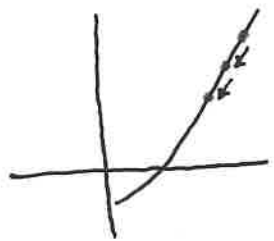

Go down (up) by small changes, check if we found zero, continue on.

Too slow. Faster way: Newton-Raphson Method.

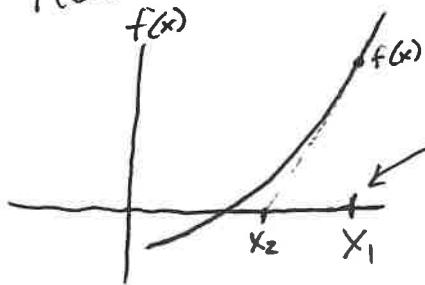Here's how it works for function $f(x) = x^3 + 2x - 2$



starting guess

Find $f(x)$

If not ≈ 0
Use slope to find next guess x_2 .


Repeat until ≈ 0

slope $f'(x)$
↳ derivative of $f(x)$

$$x_2 = x_1 - \frac{f(x_1)}{f'(x_1)}$$

⑧ Why does this work?

Start with equation to find slope.

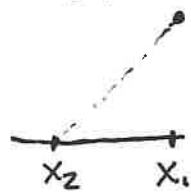

$f(x_1)$

Note $f(x_2) = 0$

$$\frac{\text{Change "y"}}{\text{Change "x"}} = \text{slope}$$

$$\frac{f(x_1) - 0}{x_1 - x_2} = \text{slope} = f'(x_1)$$

$$f(x_1) = f'(x_1) \cdot (x_1 - x_2)$$

$$\frac{f(x_1)}{f'(x_1)} = x_1 - x_2 \quad x_2 = x_1 - \frac{f(x_1)}{f'(x_1)}$$

If we have $0 = x^3 + 2x - 2$

Guess x_1

Calculate $f(x_1) = (x_1)^3 + 2(x_1) - 2$

Need to know slope $f'(x)$.

Many functions have known derivatives.

Look-up Wolfram Alpha Calculus Class


$$f(x) = x^3 + 2x - 2 \quad f'(x) = 3x^2 + 2$$

Plug in x_1 & calculate

$$x_2 = x_1 - \frac{(x_1)^3 + 2 \cdot (x_1) - 2}{3(x_1)^2 + 2}$$

⑧ Newton Raphson.m

Back to our circuit.

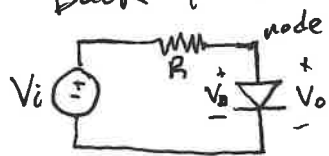


$$\frac{V_i - V_0}{R} = I_s \left(e^{\frac{V_0}{nV_T}} - 1 \right)$$

$$\frac{V_i}{R} = I_s \left(e^{\frac{V_0}{nV_T}} - 1 \right) + \frac{V_0}{R}$$

$$0 = I_s \left(e^{\frac{V_0}{nV_T}} - 1 \right) + \frac{V_0}{R} - \frac{V_i}{R}$$

$$f(V_0) = I_s \left(e^{\frac{V_0}{nV_T}} - 1 \right) + \frac{V_0}{R} - \frac{V_i}{R}$$
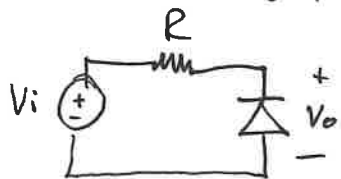
$$f'(V_0) = \frac{I_s}{nV_T} \left(e^{\frac{V_0}{nV_T}} \right) + \frac{1}{R}$$




$$V_0 = -V_D \quad V_D = -V_0$$

$$\frac{V_i - V_0}{R} = -I_s \left(e^{\frac{V_0}{nV_T}} - 1 \right)$$

$$f(x) = -I_s \left(e^{\frac{-V_0}{nV_T}} - 1 \right) + \frac{V_0}{R} - \frac{V_i}{R}$$
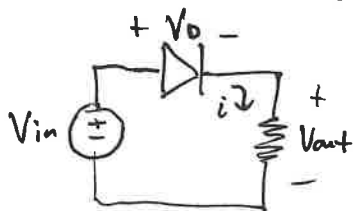
$$f'(x) = +\frac{I_s}{nV_T} \left(e^{\frac{-V_0}{nV_T}} \right) + \frac{1}{R}$$



$$V_{in} = V_D + V_{out}$$

$$V_{out} = V_{in} - V_D$$

$$\text{Current } i = \frac{V_{out}}{R} \quad i = I_s \left(e^{\frac{V_D}{nV_T}} - 1 \right)$$

$$\text{Set equal } \frac{V_{out}}{R} = I_s \left(e^{\frac{V_D}{nV_T}} - 1 \right)$$


$$\frac{V_{in} - V_D}{R} = I_s \left(e^{\frac{V_D}{nV_T}} - 1 \right)$$

$$0 = I_s \left(e^{\frac{V_D}{nV_T}} - 1 \right) + \frac{V_D}{R} - \frac{V_{in}}{R} \quad f'(x) = \frac{I_s}{nV_T} \left(e^{\frac{V_D}{nV_T}} \right) + \frac{1}{R}$$

$$\text{at end } V_{out} = V_{in} - V_D$$

9

10

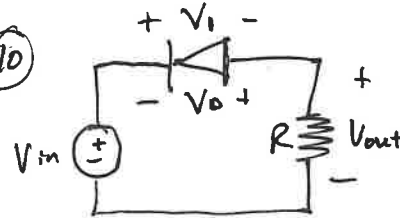

$$V_1 = -V_D$$

$$V_{out} = V_{in} - V_1$$

$$i = \frac{V_{out}}{R}$$


$$i = -I_s \left(e^{\frac{-V_1}{nV_T}} - 1 \right)$$

$$\frac{V_{out}}{R} = -I_s \left(e^{\frac{-V_1}{nV_T}} - 1 \right)$$

$$\frac{V_{in} - V_1}{R} = -I_s \left(e^{\frac{-V_1}{nV_T}} - 1 \right)$$

$$0 = -I_s \left(e^{\frac{-V_1}{nV_T}} - 1 \right) + \frac{V_1}{R} - \frac{V_{in}}{R}$$
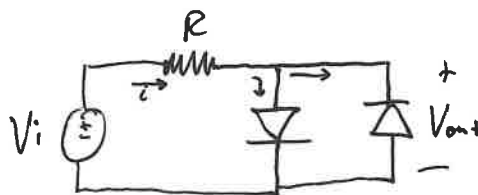
$$f'(V_1) = \frac{I_s}{nV_T} \left(e^{\frac{-V_1}{nV_T}} \right) + \frac{1}{R}$$



Current i split across diodes.

$$\frac{V_i - V_0}{R} = I_s \left(e^{\frac{V_0}{nV_T}} - 1 \right) + -I_s \left(e^{\frac{-V_0}{nV_T}} - 1 \right)$$

$$f(x) = I_s \left(e^{\frac{V_0}{nV_T}} - 1 \right) + -I_s \left(e^{\frac{-V_0}{nV_T}} - 1 \right) + \frac{V_0}{R} - \frac{V_i}{R}$$

$$f'(x) = \frac{I_s}{nV_T} \left(e^{\frac{V_0}{nV_T}} \right) + \frac{I_s}{nV_T} \left(e^{\frac{-V_0}{nV_T}} \right) + \frac{1}{R}$$


Note instead of $I_s \left(e^{\frac{V_0}{nV_T}} - 1 \right) + -I_s \left(e^{\frac{-V_0}{nV_T}} - 1 \right)$

we can use $2 I_s \cdot \sinh \left(\frac{V_0}{nV_T} \right)$

Derivative $2 \frac{I_s}{nV_T} \cosh \left(\frac{V_0}{nV_T} \right)$

If diode are assumed to be identical

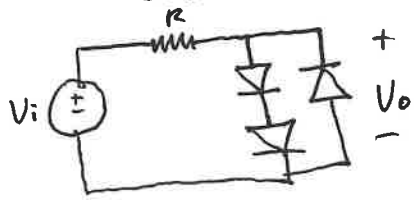Asymmetrical Distortion even & odd harmonics



2 diodes in series
same direction
1 diode in parallel
opposite direction.


~~$i = I_s(e^{\frac{V_o}{2nV_T}} - 1)$~~
 $i = I_s(e^{\frac{V_o}{2nV_T}} - 1)$
 ↑ when there are 2 diodes.

$$f(x) = I_s(e^{\frac{V_o}{2nV_T}} - 1) - I_s(e^{-\frac{V_o}{nV_T}} - 1) + \frac{V_o}{R} - \frac{V_i}{R}$$

$$f'(x) = \frac{I_s}{2nV_T} e^{\frac{V_o}{2nV_T}} + \frac{I_s}{nV_T} (e^{-\frac{V_o}{nV_T}}) + \frac{1}{R}$$


Other options: use germanium & silicon together.

Using diodes and capacitors together.

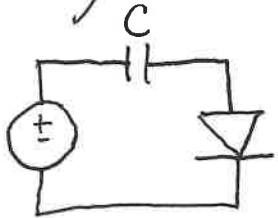

Weird circuit. Introduces
DC offset (negative)

Make DK substitution

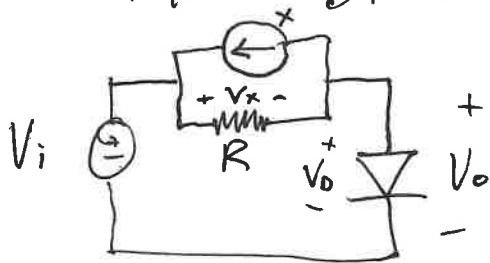

$$V_o = V_b$$

$$R = \frac{T_s}{2 \cdot C}$$

$x \rightarrow$ state variable

(11)

(12)

Current through diode
 $i = I_s(e^{\frac{V_d}{nV_T}} - 1)$

Current through capacitor
 $i = \frac{V_i - V_d}{R} - x[n-1]$

~~$\frac{V_i - V_d}{R} - x = I_s(e^{\frac{V_d}{nV_T}} - 1)$~~
 $\frac{V_i - V_d}{R} - x = I_s(e^{\frac{V_d}{nV_T}} - 1)$

$$0 = I_s(e^{\frac{V_d}{nV_T}} - 1) + \frac{V_d}{R} + x - \frac{V_i}{R}$$


$$f'(x) = \frac{I_s}{nV_T} (e^{\frac{V_d}{nV_T}}) + \frac{1}{R}$$

$$V_d[n+1] = V_d[n] - \frac{f(V_d)}{f'(V_d)}$$

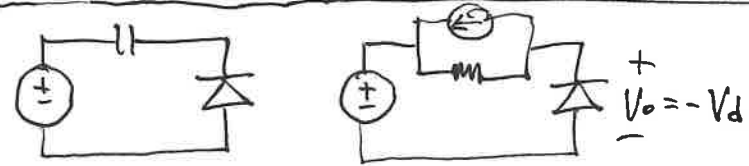(10)
diode capacitor

State update equation

$$x[n] = \frac{2}{R} (V_i - V_d) - x[n-1]$$




$$\frac{V_i - V_o}{R} - x = -I_s(e^{-\frac{V_o}{nV_T}} - 1)$$

$$0 = -I_s(e^{-\frac{V_o}{nV_T}} - 1) + \frac{V_o}{R} + x - \frac{V_i}{R}$$

$$f'(x) = \frac{I_s}{nV_T} (e^{-\frac{V_o}{nV_T}}) + \frac{1}{R}$$


$$x[n] = \frac{2}{R} (V_i - V_o) - x[n-1]$$

RC Filter with Diode.

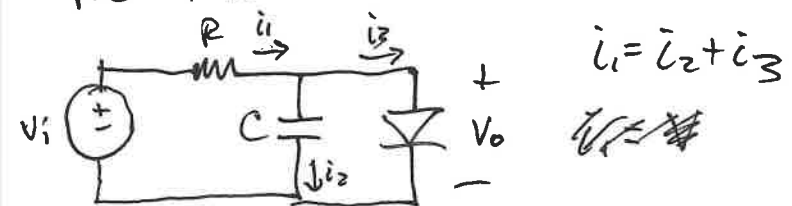

$$i_1 = i_2 + i_3$$

$$V_i = V_o$$

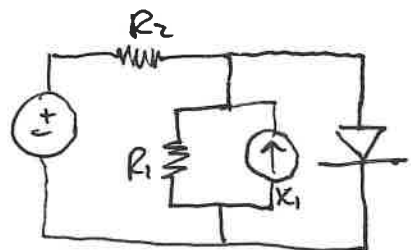

$$i_1 = \frac{V_i - V_o}{R_2}$$

$$i_2 = \frac{V_o}{R_1} - X_1$$

$$i_3 = I_s \left(e^{\frac{V_o}{nV_T}} - 1 \right)$$



$$\frac{V_i - V_o}{R_2} = \frac{V_o}{R_1} - X_1 + I_s \left(e^{\frac{V_o}{nV_T}} - 1 \right)$$

$$0 = V_o \left(\frac{1}{R_1} + \frac{1}{R_2} \right) - X_1 + I_s \left(e^{\frac{V_o}{nV_T}} - 1 \right) - \frac{V_i}{R_2}$$

$$f'(V_o) = \left(\frac{1}{R_1} + \frac{1}{R_2} \right) + \frac{I_s}{nV_T} \left(e^{\frac{V_o}{nV_T}} \right)$$

$$X_1[n] = \frac{2}{R_1} V_o - X_1[n-1]$$

RC Filter with parallel diodes

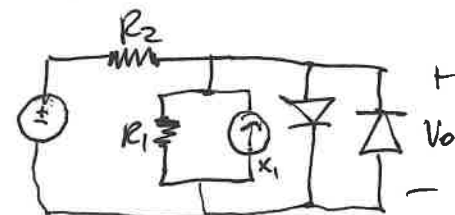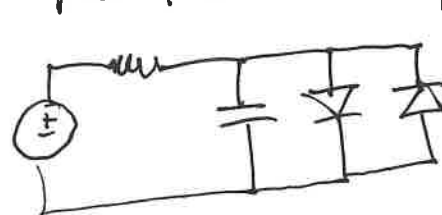


$$\text{Recall } 2 \cdot I_s \cdot \sinh\left(\frac{V_d}{nV_T}\right)$$

$$\frac{V_i - V_o}{R_2} = \frac{V_o}{R_1} - X_1 + 2 \cdot I_s \cdot \sinh\left(\frac{V_d}{nV_T}\right)$$

$$0 = \left(\frac{1}{R_1} + \frac{1}{R_2} \right) V_o - X_1 + 2 I_s \cdot \sinh\left(\frac{V_d}{nV_T}\right) - \frac{V_i}{R_2}$$

$$f''(x) = \left(\frac{1}{R_1} + \frac{1}{R_2} \right) V_o + \frac{2 I_s}{nV_T} \cdot \cosh\left(\frac{V_d}{nV_T}\right)$$
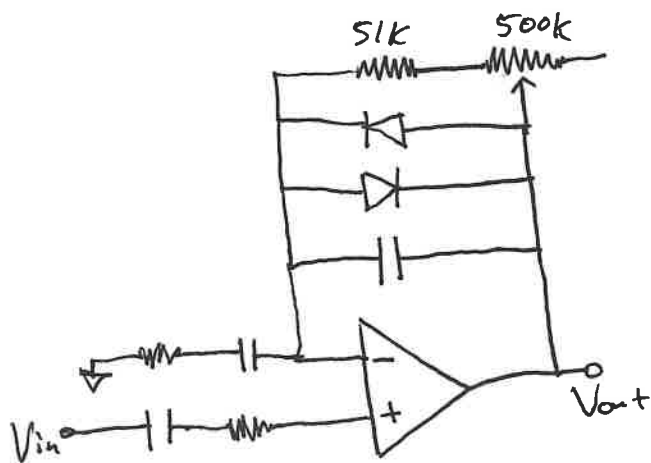
$$X_1[n] = \frac{2}{R_1} \cdot V_o - X_1[n-1]$$




Notes: no current can flow into "+" terminal of op-amp. As a result, there is no voltage drop across input R & C.
Node at input to op-amp = V_{in} .

* The op-amp is an important buffer for this sub-circuit in the context of the entire circuit. However, for our model we can actually work without it.

* We can replace the two diodes with a single block. $i = 2I_s \cdot \sinh\left(e^{\frac{V_d}{nV_T}}\right)$

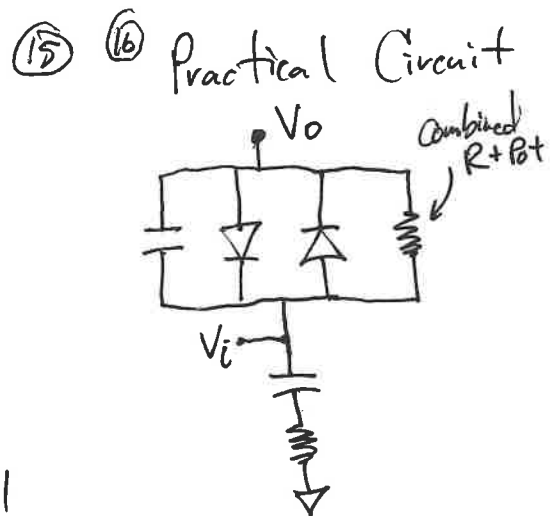* The potentiometer is in series with 51k resistor. Combined they have a resistance between 51k - 551k



Voltage Divider

$$V_o = V_d + V_i$$

Voltage across 3 parallel components.

Use voltage ~~across~~ across diode for all

$$V_{R2} = V_d = V_{R3}$$

Total current


$$i = i_2 + i_d + i_3$$

$$i_2 = \frac{V_{R2}}{R_2} - X_2 = \frac{V_d}{R_2} - X_2$$

$$i_3 = \frac{V_{R3}}{R_3} = \frac{V_d}{R_3} \quad i_d = 2 \cdot I_s \cdot \sinh\left(\frac{V_d}{nV_T}\right)$$

$$i = \frac{V_d}{R_2} - X_2 + 2 \cdot I_s \cdot \sinh\left(\frac{V_d}{nV_T}\right) + \frac{V_d}{R_3}$$

Save for later.

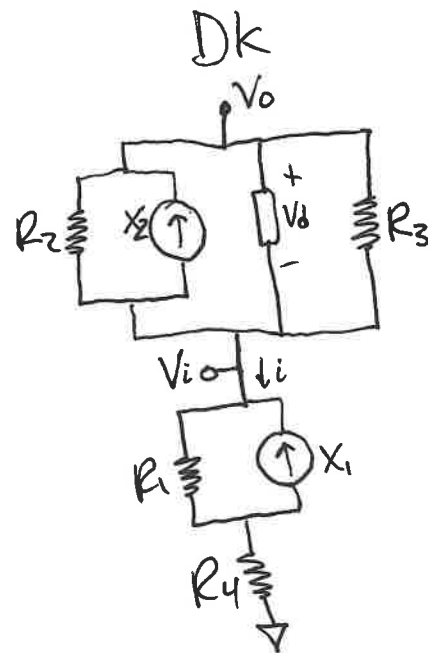

$V_i = V_{R1} + V_{R4}$
 Currents must be equal through R & C

$$\frac{V_{R4}}{R_4} = \frac{V_{R1}}{R_1} - X_1 \quad \text{Solve for } \frac{V_{R4}}{R_4} \text{ and replace}$$

$$\frac{V_{R4}}{R_4} + X_1 = \frac{V_{R1}}{R_1} \Rightarrow \frac{R_1}{R_4} V_{R4} + R_1 X_1 = V_{R1}$$

$$V_i = \frac{R_1}{R_4} V_{R4} + R_1 X_1 + V_{R4} \quad \text{Solve for } \frac{V_{R4}}{R_4} \text{ and replace}$$

$$V_i - R_1 X_1 = V_{R4} \left(\frac{R_1}{R_4} + 1 \right)$$

$$V_{R4} = \frac{V_i}{G_4} - \frac{R_1}{G_4} X_1 \quad \text{Plug back in}$$

$$i = \frac{V_{R4}}{R_4} \quad i = \frac{V_i}{G_4 R_4} - \frac{R_1}{G_4 R_4} X_1$$

Current in bottom of circuit must equal current in top.

$$\frac{V_i}{G_4 R_4} - \frac{R_1}{G_4 R_4} X_1 = \frac{V_d}{R_2} - X_2 + \frac{V_d}{R_3} + 2 \cdot I_s \cdot \sinh\left(\frac{V_d}{nV_T}\right)$$

$$0 = \frac{-V_i}{G_4 R_4} + \frac{R_1}{G_4 R_4} X_1 + \frac{V_d}{R_2} - X_2 + \frac{V_d}{R_3} + 2 \cdot I_s \cdot \sinh\left(\frac{V_d}{nV_T}\right)$$

$$f'(V_d) = \frac{1}{R_2} + \frac{1}{R_3} + \frac{2 \cdot I_s}{nV_T} \sinh\left(\frac{V_d}{nV_T}\right)$$

Use in Newton solver for V_d . Then $V_{out} = V_d + V_{in}$

⑬ ⑭ State Update Equations.

$$X_2[n] = \frac{2}{R_2} \cdot V_{R2} - X_2[n-1] = \frac{2}{R_2} V_d - X_2[n-1]$$

$$X_1[n] = \frac{2}{R_1} V_{R1} - X_1[n-1]$$

$$V_i = V_{R1} + V_{R4} \quad \leftarrow \text{replace } V_{R4} \text{ so everything is a function of } V_{R1}$$

$$\frac{V_{R4}}{R_4} = \frac{V_{R1}}{R_1} - X_1$$

$$V_{R4} = \frac{R_4}{R_1} V_{R1} - X_1 \cdot R_4$$

$$V_i = V_{R1} + \frac{R_4}{R_1} V_{R1} - R_4 X_1 \quad \text{isolate } V_{R1}$$

$$V_i + R_4 X_1 = V_{R1} \left(1 + \frac{R_4}{R_1} \right)$$

$$V_{R1} = \frac{V_i}{G_1} + \frac{R_4}{G_1} X_1 \quad \text{Plug in state equation}$$

$$X_1[n] = \frac{2}{R_1} \left[\frac{V_i}{G_1} + \frac{R_4}{G_1} X_1 \right] - X_1$$